

Carleton University  
ELEC 4609A: Integrated Circuit Design and Fabrication  
Static Logic PRSG Project Report  
Group 19

Hussin Abdullah (101155276) & Theo Cens (101105855)  
December 8th, 2023


## Table of Contents

<b>Chapter 1: IC Project Design.....</b>	<b>3</b>
1.0 INTRODUCTION.....	3
2.0 SYSTEM DESIGN.....	4
3.0 DESIGN OF INDIVIDUAL BLOCKS.....	5
3.1 Inverter.....	5
3.2 NAND Gate.....	7
3.3 NOR Gate.....	9
3.4 XNOR Gate.....	11
3.7 Master Clock Generator.....	13
3.6 D Flip-Flop.....	15
3.7 Output Driver.....	17
4.0 HIGH LEVEL DISCUSSION.....	19
4.1 Input Protection.....	19
4.2 PRSG.....	20
4.3 Top Level.....	22
<b>Chapter 2: IC Project Testing.....</b>	<b>24</b>
1.0 INTRODUCTION.....	24
1.1 Measured Results.....	27
2.0 TEST RESULTS.....	28
<b>Chapter 3: Op-Amp Layout Project.....</b>	<b>30</b>
1.0 INTRODUCTION.....	30
2.0 SCHEMATIC SIMULATION.....	32
3.0 OP-AMP LAYOUT.....	49
4.0 LAYOUT SIMULATION.....	52
<b>Chapter 4: Group Member Contributions.....</b>	<b>54</b>
1.0 CuSOI Schematics & Simulation:.....	54
2.0 CuSOI Layout.....	54
3.0 CuSOI Report.....	54
4.0 OpAmp Schematics & OpAmp PVT Simulations.....	54
5.0 OpAmp Layout.....	54
6.0 OpAmp Report.....	54
7.0 General Report Writing.....	54




## 2.0 SYSTEM DESIGN

The chip will produce a bit stream that appears random, but will repeat every 31 bits. Figure 1.2 shows a high level PRSG logic block diagram of the heart of the chip. There are five D flip flops and one XNOR gate with reset. It is also expected that the clock be generated using a master clock generator within the chip. This design is being used because it doesn't require a 2-phase clock generator and the d flip flops are not sensitive to off state leakage problems.

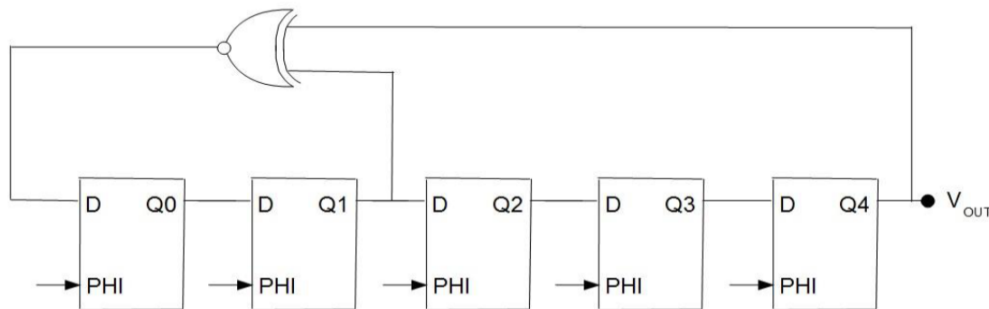


**Figure 1.2:** Pseudorandom sequence generator implemented with shift register and feedback.

Figures 1.3 and 1.4 show the XNOR gate with reset and the D flip flop.

 

**Figure 1.3:** XNOR gate design with reset.

 

**Figure 1.4:** D flip flop design.



### 3.0 DESIGN OF INDIVIDUAL BLOCKS


#### 3.1 Inverter

Inverters are NOT gates that will invert the input signals. Table 2 shows the expected output from all possible inputs. Note that the gate will have an inherent delay, so two inverters in series can act as a buffer.

**Table 2:** NAND gate truth table.


A	OUT
0	1
1	0

Figure 1.5 shows the inverter schematic design. The pmos has a length to width ratio of 0.25 and the nmos has a ratio of 0.50. The minimum wire width is set at 4.8 and the measurements must be in increments of 2.4u. Therefore, the pmos has a length of 4.8u and a width of 19.2u. The nmos has a length of 4.8u and a width of 9.6u.

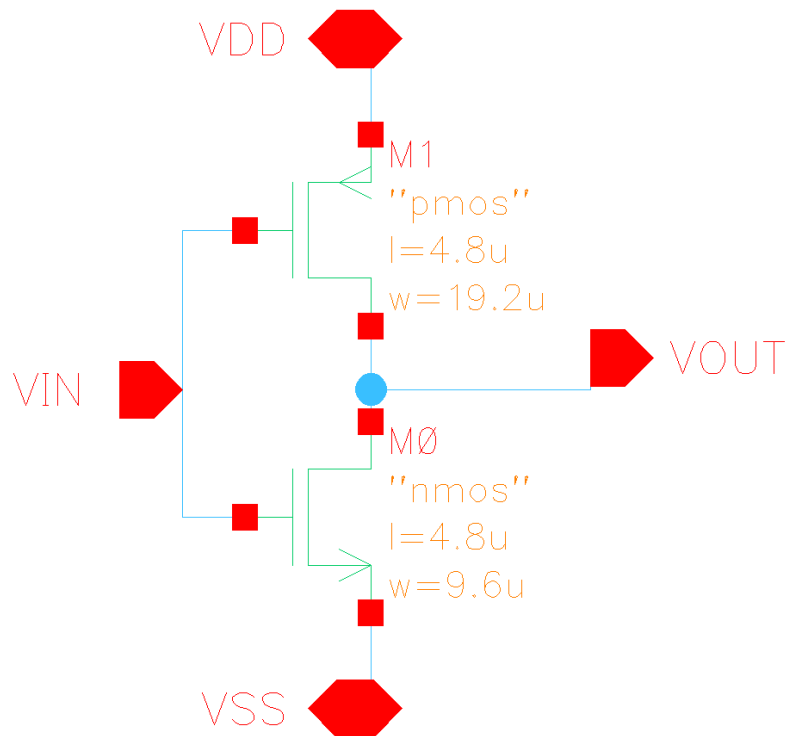


**Figure 1.5:** Inverter schematic design

Figure 1.6 shows the simulation results of the inverter schematic. These results are found to be successful. The pull-down time is 1ns and the pull-up time is 2 ns. Before the signals stabilise, the voltage peaks to well above the input values.

 

**Figure 1.6:** Inverter schematic simulation.

Figure 1.7 shows the inverter layout design. Since this gate is versatile and simple, multiple configurations were created to fit awkward space to maximise space. This layout is from the master clock generator.

 

**Figure 1.7:** Inverter layout design.


### 3.2 NAND Gate

NAND gates will only output low if both inputs are high. Table 3 shows the expected output from all possible inputs.

**Table 3:** NAND gate truth table.


A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

Figure 1.8 shows the NAND gate schematic design. Each pmos has a length to width ratio of 0.25 and the nmos has a ratio of 0.25. The minimum wire width is set at 4.8 and the measurements must be in increments of 2.4u. Therefore, the pmos have a length of 4.8u and a width of 19.2u. The nmos have a length of 4.8u and a width of 19.2u.

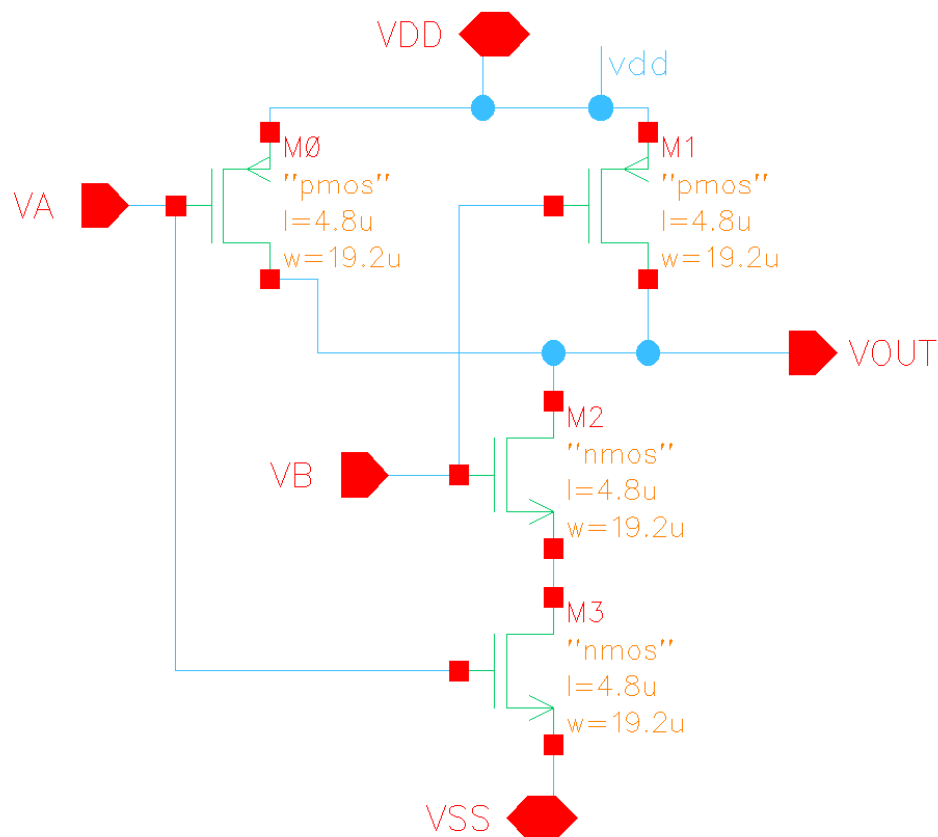


**Figure 1.8:** NAND gate schematic

Figure 1.9 shows the simulation results of the NAND gate schematic. These results are found to be successful. The pull-down time is 5ns and the pull-up time is 7ns. Before the signals stabilise, the voltage peaks to well above the input values.

 

**Figure 1.9:** NAND gate schematic simulation results.

Figure 1.10 shows the NAND gate layout design. This layout is used throughout the chip.

 

**Figure 1.10:** NAND gate layout design.


### 3.3 NOR Gate

NOR Gates will only output high if both inputs are low. Table 4 shows the expected output from all possible inputs.

**Table 4:** NOR gate truth table.


A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	0

Figure 1.11 shows the NOR gate schematic design. Each pmos has a length to width ratio of 0.125 and the nmos has a ratio of 0.50. The minimum wire width is set at 4.8 and the measurements must be in increments of 2.4u. Therefore, the pmos have a length of 4.8u and a width of 38.4u. The nmos have a length of 4.8u and a width of 9.6u.

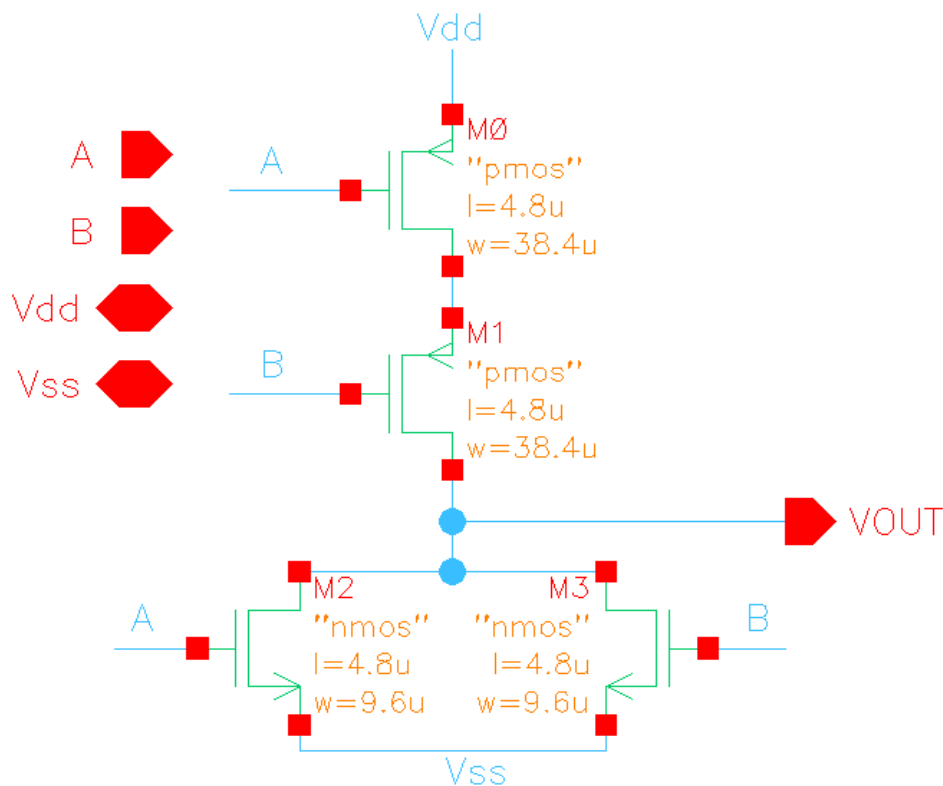


**Figure 1.11:** NOR gate schematic design.

Figure 1.12: shows the simulation results of the NOR gate schematic. These results are found to be successful. The pull-down time is 1ns and the pull-up time is 6ns. Before the pull-down signal stabilises, the voltage peaks to well above the input values.

 

**Figure 1.12:** NOR gate schematic simulation results.

Figure 13 shows the NOR gate layout design. Note that this gate layout is larger and only used once, in the XNOR gate.

 

**Figure 1.13:** NAND gate layout design.


### 3.4 XNOR Gate

XNOR Gates will only output high if both inputs are equal. This gate also requires a reset that will output low when the reset is high. Table 5 shows the expected output from all possible inputs.

**Table 5:** NOR Gate truth table.


RST	A	B	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Figure 1.14 shows the XNOR gate schematic design. It incorporates four NAND gates and a NOR gate for the reset.

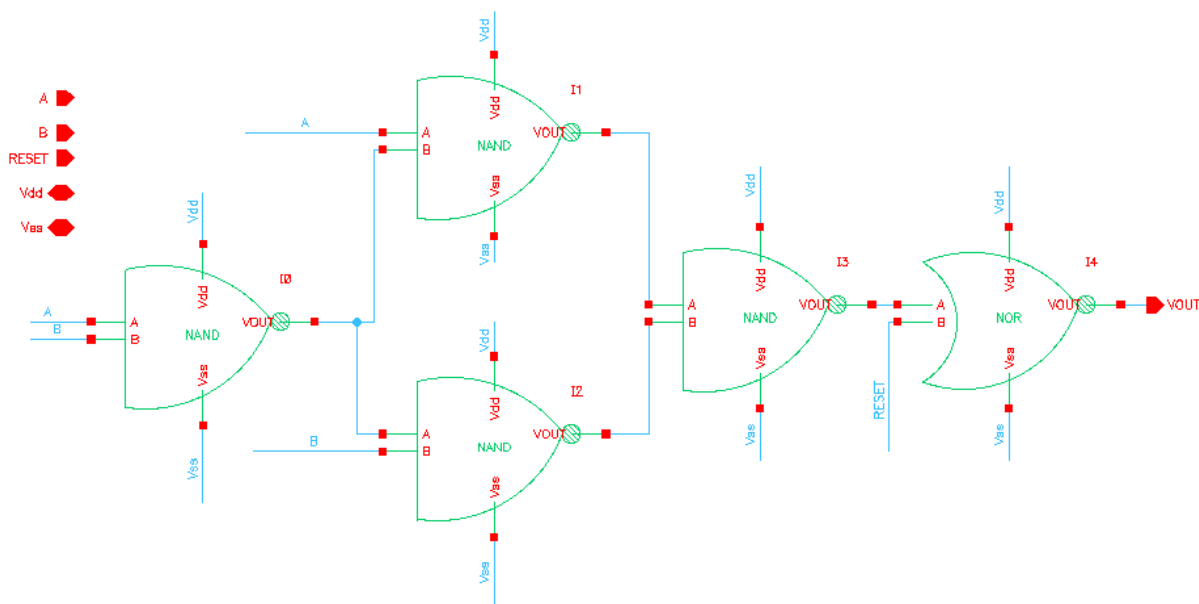


**Figure 1.14:** XNOR Gate schematic design.

Figure 1.15 shows the simulation results of the XNOR gate schematic. These results are found to be successful. The pull-down time is 11ns and the pull-up time is 12ns. Before the pull-up signal stabilises, the voltage peaks to well above the input values.

 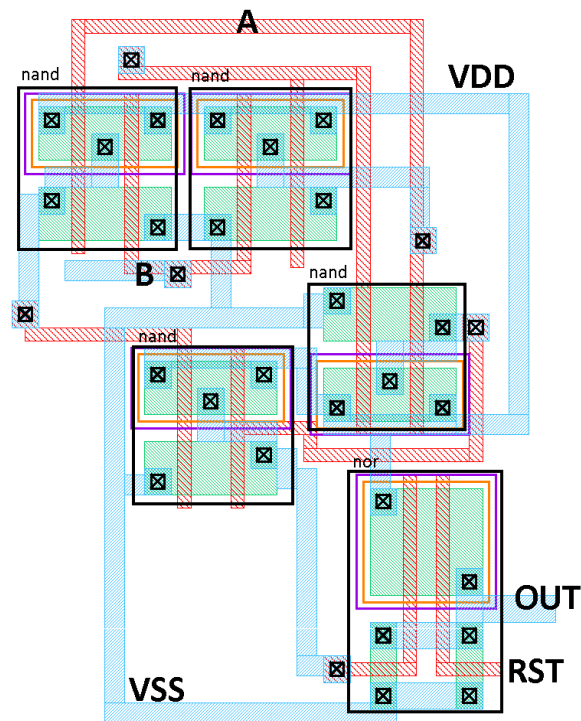

**Figure 1.15:** XNOR Gate schematic simulation results.

Figure 1.16 shows the XNOR gate layout design. The XNOR gate is the largest, and in this example, is even larger than the D Flip Flop. The size is not optimised because there was enough space to include it as is. However, given more time, this design could be made smaller.

 


**Figure 1.16:** XNOR Gate layout design.




### 3.7 Master Clock Generator

 The master clock generator (oscillator) will generate the clock from an external capacitor connected across both C1 and C2 pads in the circuit. Figure 1.17 shows the master clock generator schematic design. The circuit uses four inverters and an nmos with a length of 84u and a width of 4.8u.

 


**Figure 1.17:** Master clock generator schematic design.



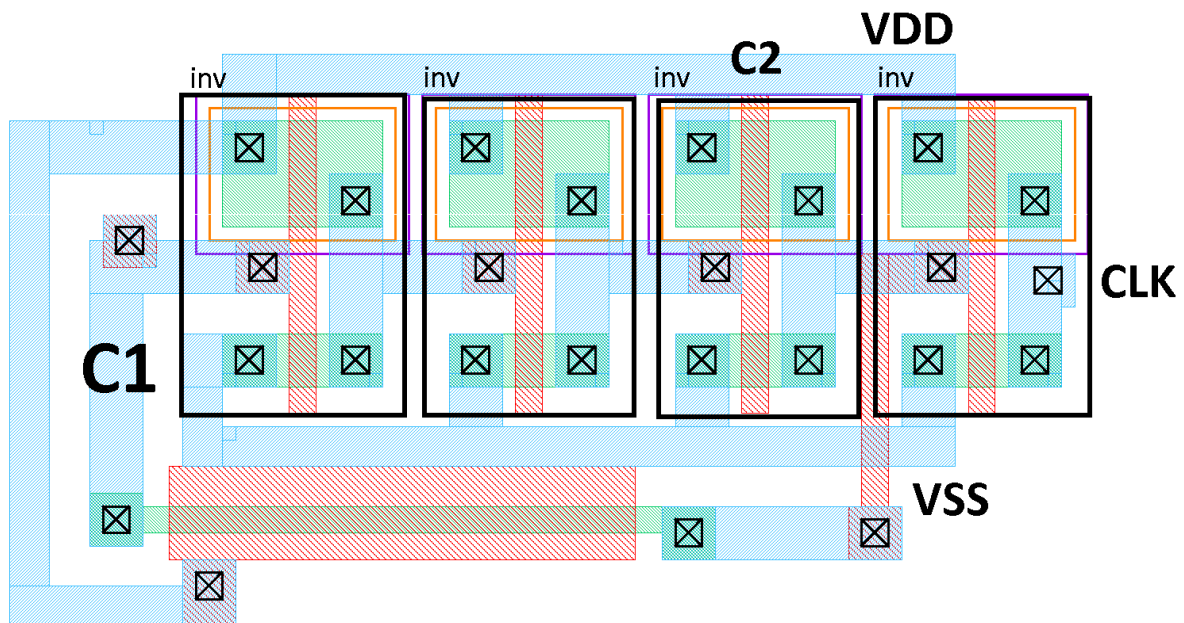
**Figure 1.18:** Testbench schematic design.

Figure 1.19 shows the simulation results of the master clock generator schematic. These results are found to be successful. The rise and fall times appear to be instantaneous.



**Figure 1.19:** Master clock generator schematic simulation results.

Figure 1.20 shows the master clock generator layout design.

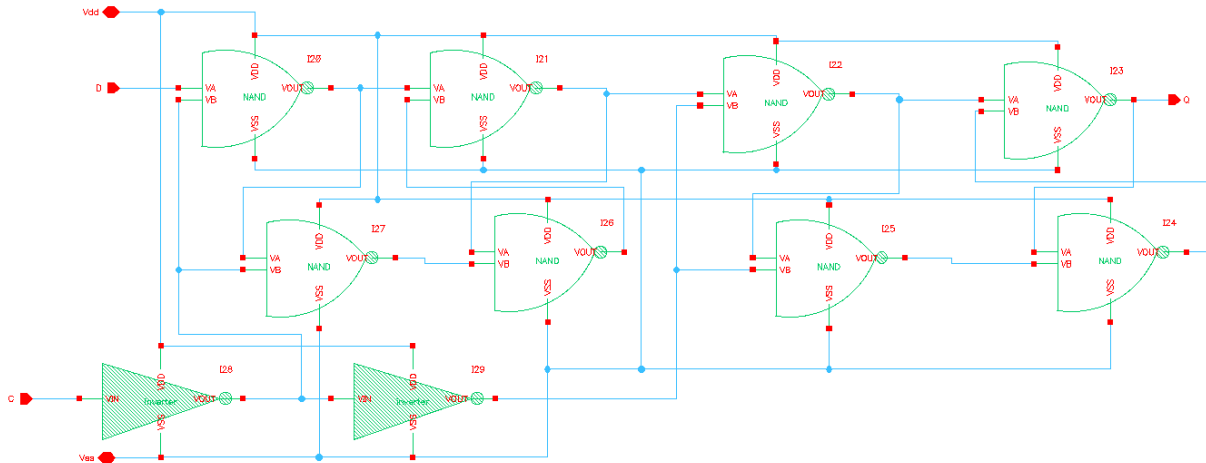


**Figure 1.20:** Master clock generator layout design.

### 3.6 D Flip-Flop


The D Flip Flop is a register that will hold the input from the rising edge of the clock.

Figure 1.21 shows the D flip flop schematic design. The circuit incorporates two latches which each have four NAND gates and one inverter.




**Figure 1.21:** D Flip Flop schematic design.

Figure 1.22 shows the simulation results of the D flip flop schematic. These results are found to be successful. The pull-up and pull-down both take 20ns to stabilise.

 

**Figure 1.22:** D Flip Flop schematic simulation results.


Figure 1.23 shows the D flip flop layout design. This layout was made as small as possible because five of them were required in the final design. The inverters were stretched along the side so that the flip flops could be stacked without wasting space. A vertical configuration was used so that three could fit together within  $240\lambda$  (the maximum height of the chip).

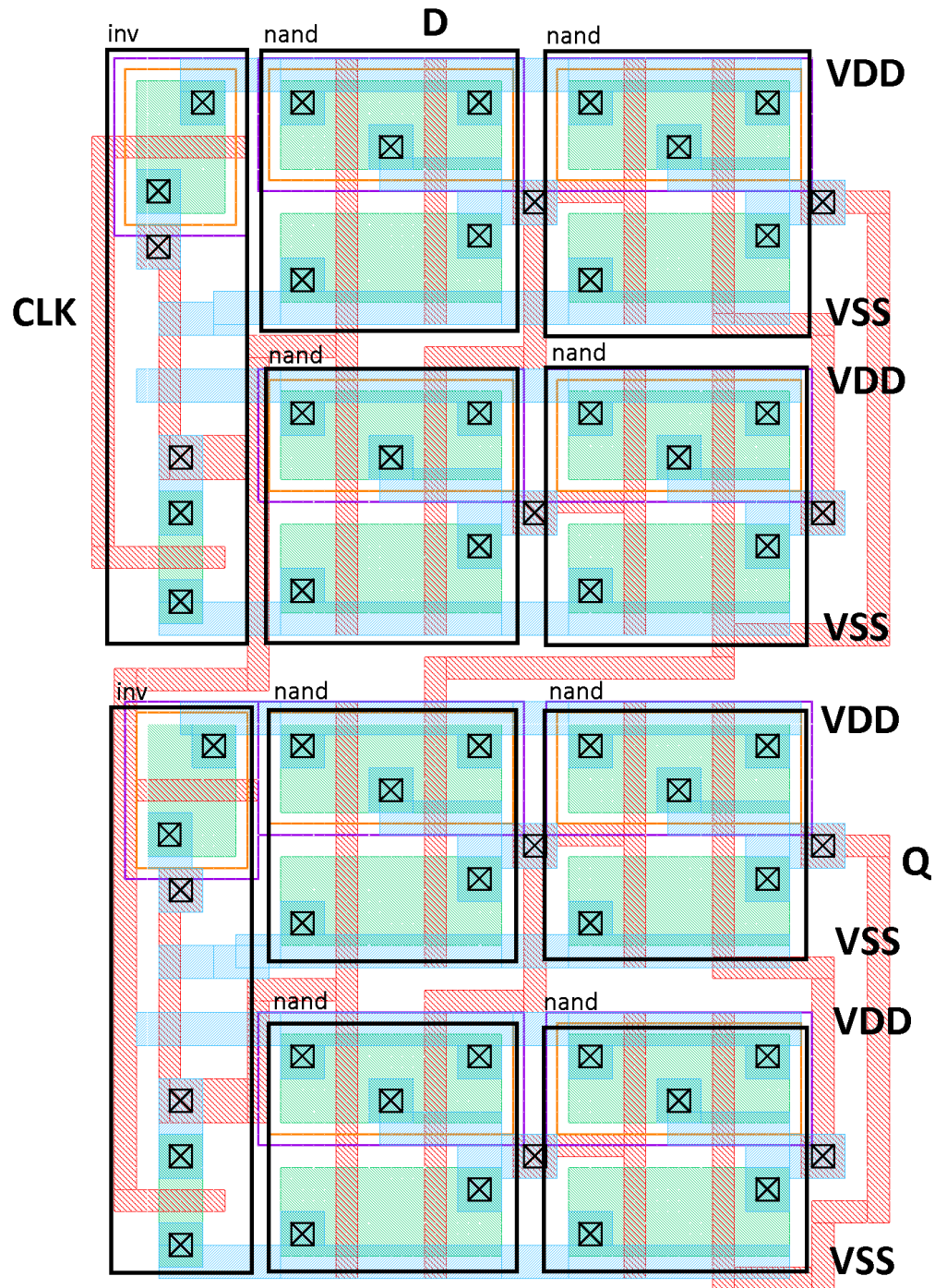

**Figure 1.23:** D Flip Flop layout design.


### 3.7 Output Driver

The output driver will be able to single 10mA of current. The output driver consists of a single wide nmos in open drain configuration connected to the VOUT minipad. An LED is also connected to it. The output driver schematic is shown in figure 1.24.

 

**Figure 1.24:** Output driver schematic design.


Figure 1.25 shows the simulation results of the output driver schematic.

 

**Figure 1.25:** Output driver schematic simulation.



Figure 1.26 shows the output driver layout design. This layout uses as many nodes as possible in order to maintain signal integrity.

 

**Figure 1.26:** Output driver layout design.

## 4.0 HIGH LEVEL DISCUSSION

### 4.1 Input Protection

The input protection is meant to protect from 1kV for 1ns. The input protection should not allow more than 50V to pass through. This means that the input protection should have a high resistance. Trial and error was used to find the width of the nmos. The length is 4.8u and the width is 180u. The input protection schematic design is shown in figure 1.27.

 


Figure 1.27: Input protection schematic design.

Figure 1.28 shows the simulation results for the input protection schematic. These results are found to be successful. The maximum voltage is under 50V.


 


Figure 1.28: Input protection schematic simulation results.


Figure 1.29 shows the input protection layout design. This layout uses one long finger rather than multiple shorter fingers, because one finger increases the resistance of the transmission. The d-well material is used because it has the highest resistance.

 

**Figure 1.29:** Input protection layout design.

## 4.2 PRSG


Figure 1.30 shows the complete PRSG schematic design. The design incorporates five D flip flops and one XNOR gate.

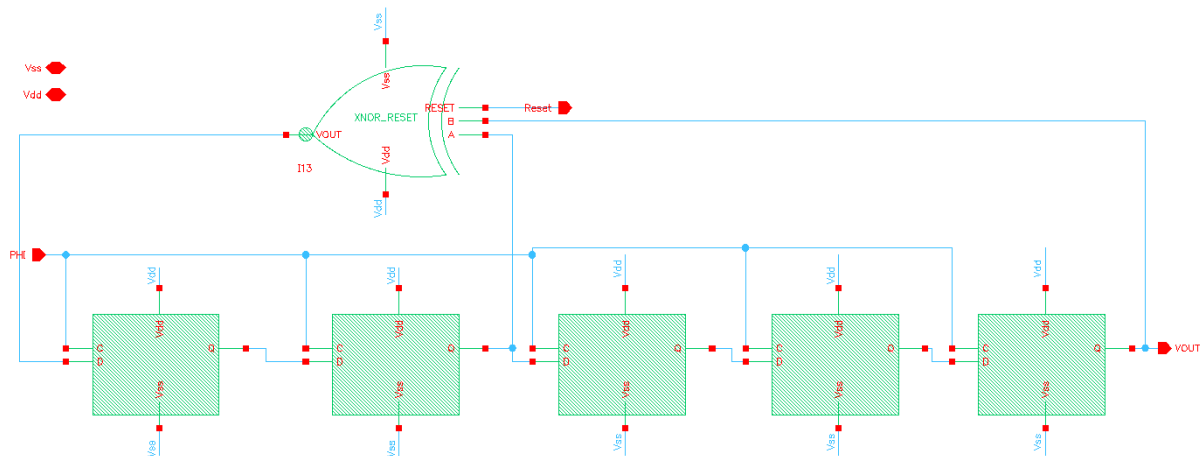 

**Figure 1.30:** PRSG schematic design.

 


Figure 1.31 shows two full cycles of the simulation results for the PRSG. These results are found to be successful



**Figure 1.31:** PRSG schematic simulation results.


Figure 1.32 shows the simulation results for the reset on the PRSG. The reset takes 3us to fully reset. These results are found to be successful



**Figure 1.32:** PRSG schematic simulation results with reset.


### 4.3 Top Level

Figure 1.33 shows the top level schematic design of the chip. The circuit incorporates inputs protections of each of the input pads (C1, C2, VIN, VDD) and an output driver on the output pad (VOUT).

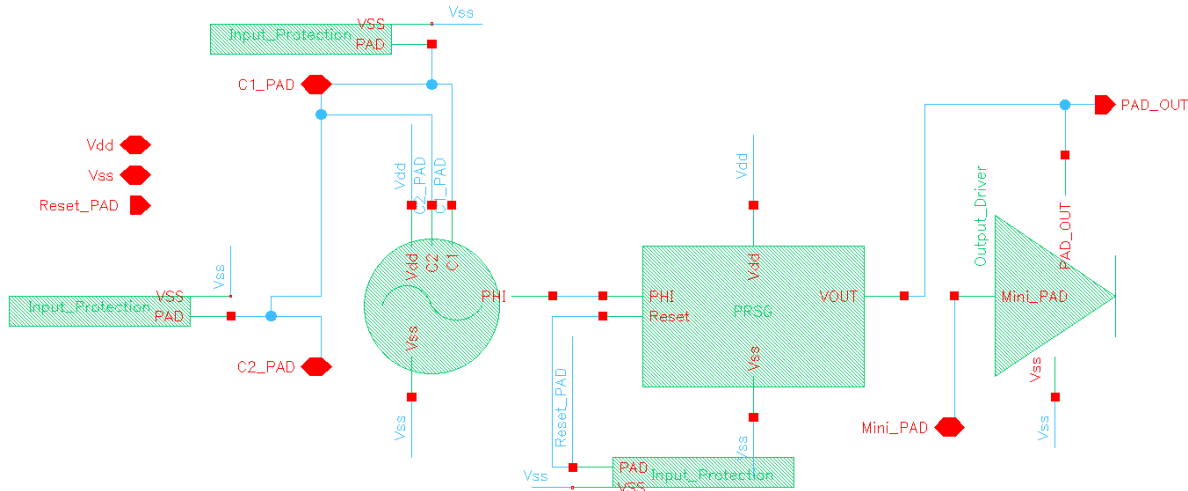

**Figure 1.33:** Top level schematic with all components.

Figure 1.34 shows the top level layout design of the chip.

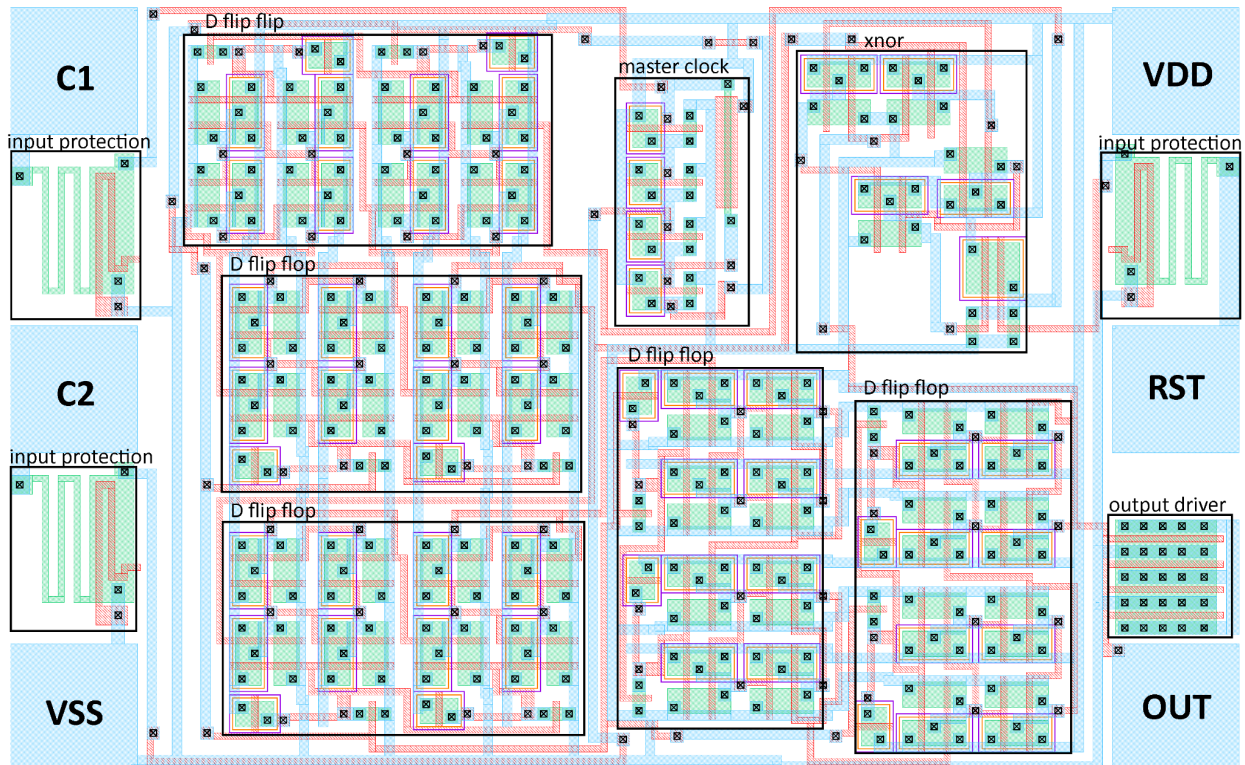

**Figure 1.34:** Top level layout design.

Figures 1.35 and 1.36 show that the layout passes LVS and DRC through due to both LVS happy face and drc.summary.

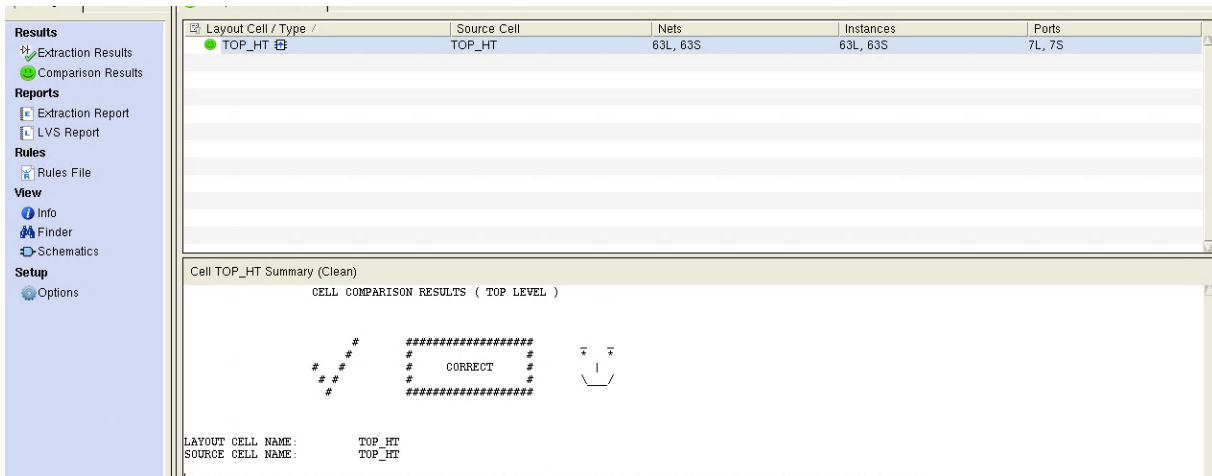


Figure 1.35: LVS pass confirmation.

```

--- RULECHECK RESULTS STATISTICS
---
RULECHECK METAL_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK METAL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK POLY_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK POLY_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK FIELD_POLY_DWELL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK FIELD_POLY_SOURCE_DRAIN_TOUCHING ..... TOTAL Result Count = 0 (0)
RULECHECK DWELL_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK DWELL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_METAL_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_POLY_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK CHANNEL_CONTACT_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_D_WELL_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK NWELL_DWELL_OVERLAP_1 ..... TOTAL Result Count = 0 (0)
RULECHECK NWELL_DWELL_OVERLAP_2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_NWELL_OVERLAP_2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_P_SOURCE_DRAIN_ENCLOSURE ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_DWELL_OVERLAP_2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_N_SOURCE_DRAIN_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE_1 ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE_2 ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE_3 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_1 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_2 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_3 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_4 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_5 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_6 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid_7 ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_METAL ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_POLY ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_DWELL ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_NPLUS ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_PPLUS ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_CONTACT ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_NWELL ..... TOTAL Result Count = 0 (0)
-----
--- RULECHECK RESULTS STATISTICS (BY CELL)
---
--- SUMMARY
---
TOTAL CPU Time: 0
TOTAL REAL Time: 0
TOTAL Original Layer Geometries: 747 (2145)
TOTAL DRC RuleChecks Executed: 36
TOTAL DRC Results Generated: 0 (0)

```


Figure 1.36: DRC summary.



## Chapter 2: IC Project Testing


### 1.0 INTRODUCTION

The testing is done using a Wentworth Probe Station and the waveforms are measured and recorded using an oscilloscope. Both fabrication and testing is done in the Carleton University Microelectronics Fabrication Facility. Figure 2.1 shows the probe station that was used with connection to the oscilloscope, capacitor, and input currents.

 

**Figure 2.1:** Photograph of chip in the Wentworth Probe Station at Carleton University.


Six probes connected to the pads of the chip. These are thin metal rods that are delicately moved to connect to the pads using Wentworth Probe Station. Figure 2.2 shows the probes connected to the pads.

 

**Figure 2.2:** Photograph through microscope of probes connected to the pads.



A 10nF capacitor is connected between pads C1 and C2. It will provide a clock frequency near 1kHz to make testing simpler. A digital oscilloscope is connected to the VOUT pad. It can also be connected to the C2 pad to test the clock cycle. Finally, an HP 4155A Semiconductor Analyzer is connected to the RESET pad. Figure 2.3 shows the completed chip.

 


**Figure 2.3:** Photograph of completed chip.

Testing Equipment Used in Lab:

- HP 4155A Semiconductor Analyzer
- Wentworth Probe Station w/ 6 Probes (5 If you built a counter)
- TekTronix TDS2024C Digital Oscilloscope


## 1.1 Measured Results

Figure 2.4 shows the measured pseudorandom output waveform. These results are found to be unsuccessful because they do not match the expected pseudorandom sequence. After some time the output remains high.

 

**Figure 2.4:** Measured pseudorandom output waveform.


Figure 2.5 shows the measured clock signal from the C2 pad as seen from the oscillator in the lab.

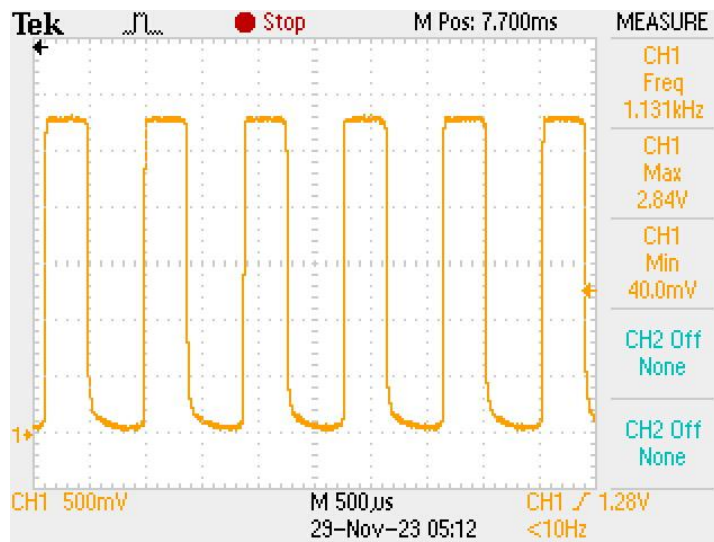

**Figure 2.5:** Measured clock signal at the C2 minipad.


## 2.0 TEST RESULTS

As shown in figure 2.6, these results are found to be successful. They are regular and consistent. The measured clock wavelength is  $0.00531 - 0.006194 = 0.884$  ms.

 

**Figure 2.6:** Measured clock signal at the C2 minipad.


As shown in figure 2.7, the expected clock wavelength is 1.11 ms. These values are close enough to count the master clock generators as successful. The reason the values are not exactly the same is because of the capacitor. Modifying the capacitor will allow for a more precise clock frequency.

 


**Figure 2.7:** Expected clock signal at the C2 minipad.



Figure 2.8 shows the measured output waveform from the oscillator during testing. Figure 2.9 shows the expected output waveform.

 

**Figure 2.8:** Measured pseudorandom output waveform.

 

**Figure 2.9:** Expected pseudo-random output waveform.

As shown above the results of the measured Pseudo-random output does not match the expected value. Since both DRC and LVS passed, then the error could be caused by one or a combination of the following:

Voltage or current tolerances of individual components were exceeded, issues with power supply and delivery into the pseudo-random sequence generator, variations in temperature, software bug or logic errors, signal integrity issues and hardware malfunctions. These hardware malfunctions could be anything from poor connections, components failing and/or improper material for components or wires.

## Chapter 3: Op-Amp Layout Project

### 1.0 INTRODUCTION

This project focuses on the design approach for a two-stage operational amplifier using a 45nm soi CMOS process. Operational-amplifiers are highly versatile components that can be utilised in many electronic systems. Initially students will begin by creating the given schematic in Cadence.

Figure 3.1 shows the Op-Amp design schematic.

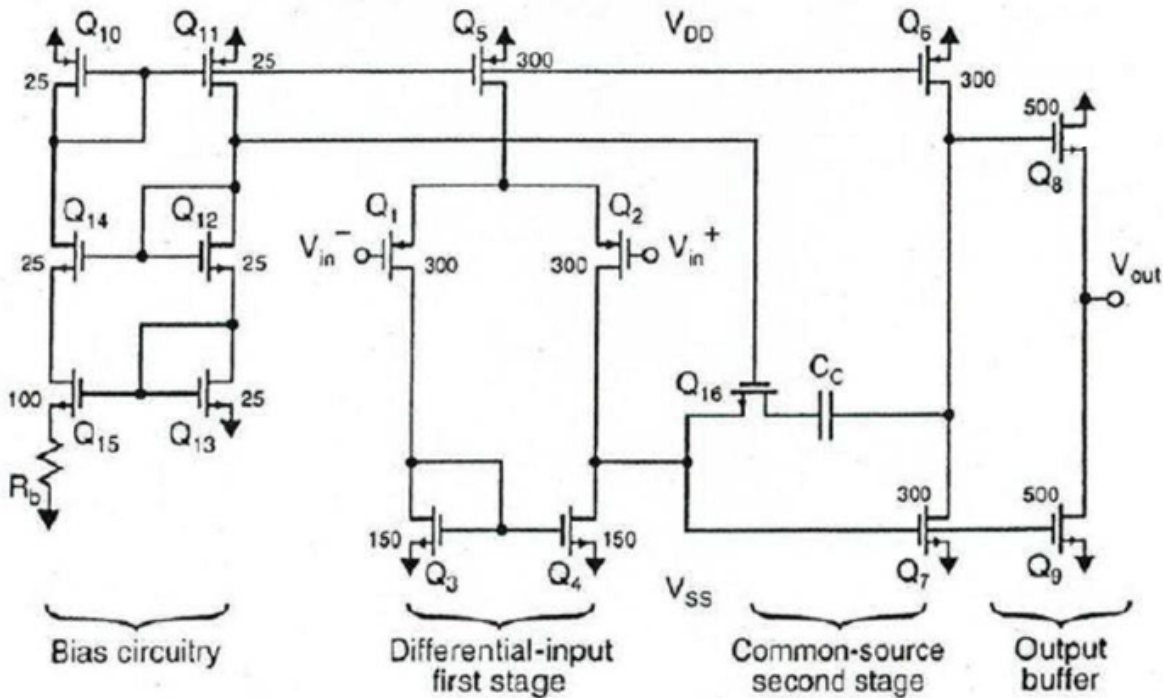


Figure 3.1: Op-Amp design schematic.

Using the schematic made in Cadence, we will initially simulate the operational amplifier under nominal conditions. Following this we will again simulate the schematic however varying the Processes, Voltages and Temperature. A total of 27 sets of data will be accrued. After getting a good understanding of the operational amplifier through the simulations, we design a top level layout floor plan based on the transistor dimensions that are provided below.


**Table 6:** Given transistor ratios and fingers.

Transistor	Type	(W/L)	Length (nm)	Width (um)	Fingers
Q1	P	300	40	12	6
Q2	P	300	40	12	6
Q3	N	150	40	6	3
Q4	N	150	40	6	3
Q5	P	300	40	12	6
Q6	P	300	40	12	6
Q7	N	300	40	12	6
Q8	N	2500	40	100	50
Q9	N	2500	40	100	50
Q10	P	25	40	1	1
Q11	P	25	40	1	1
Q12	N	25	40	1	1
Q13	N	25	40	1	1
Q14	N	25	40	1	1
Q15	N	100	40	4	2
Q17	N	25	40	1	1


Finally with the top level layout floor plan complete the final step is to create the layout view using the floorplan created. Extracting the layout view we will simulate the schematic vs extracted view for various cases.

## 2.0 SCHEMATIC SIMULATION

In cadence the schematic was created based on the given parameters. Following this the following results were obtained. Figures 3.2 and 3.3 show both the schematic design and testbench design.

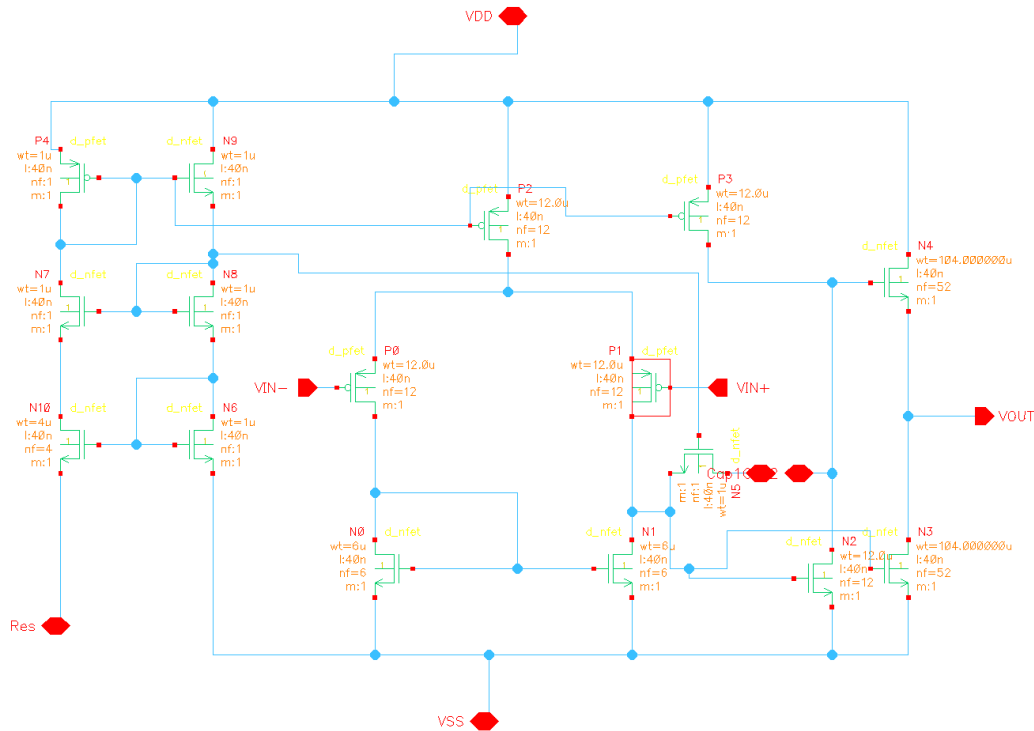

**Figure 3.2:** Operational Amplifier Schematic in Cadence.

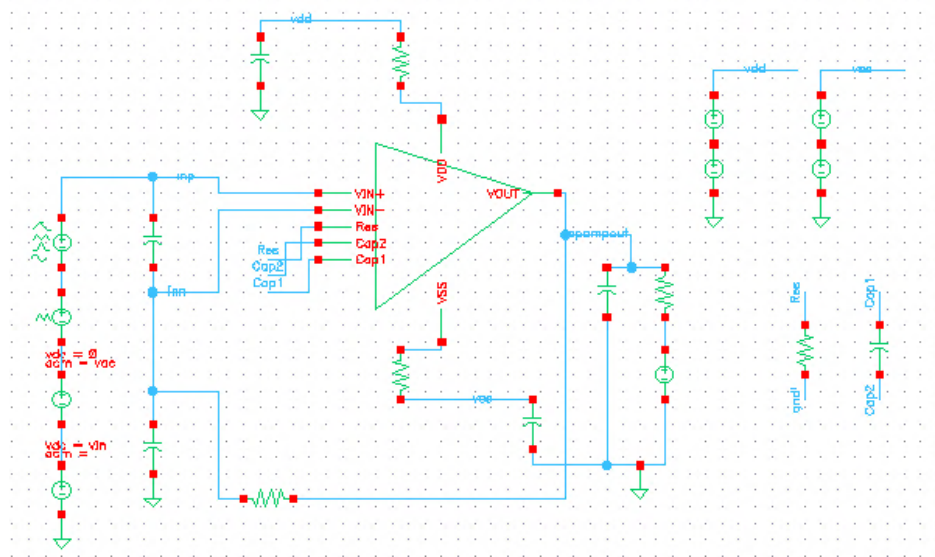

**Figure 3.3:** Testbench Operational Amplifier Schematic in Cadence.

Beginning with simulations under nominal conditions (NN, 1.2V, 25°C):

**Open Loop Gain:**  
20.38

 


Figure 3.4: Open loop gain under normal conditions.

**Unity Gain Bandwidth:**  
2.043MHz

 


Figure 3.5: Unity gain bandwidth under normal conditions.

Phase Margin:  
110.8°

 


Figure 3.6: Phase margin under normal conditions.

Power Dissipation:  
864.8uW

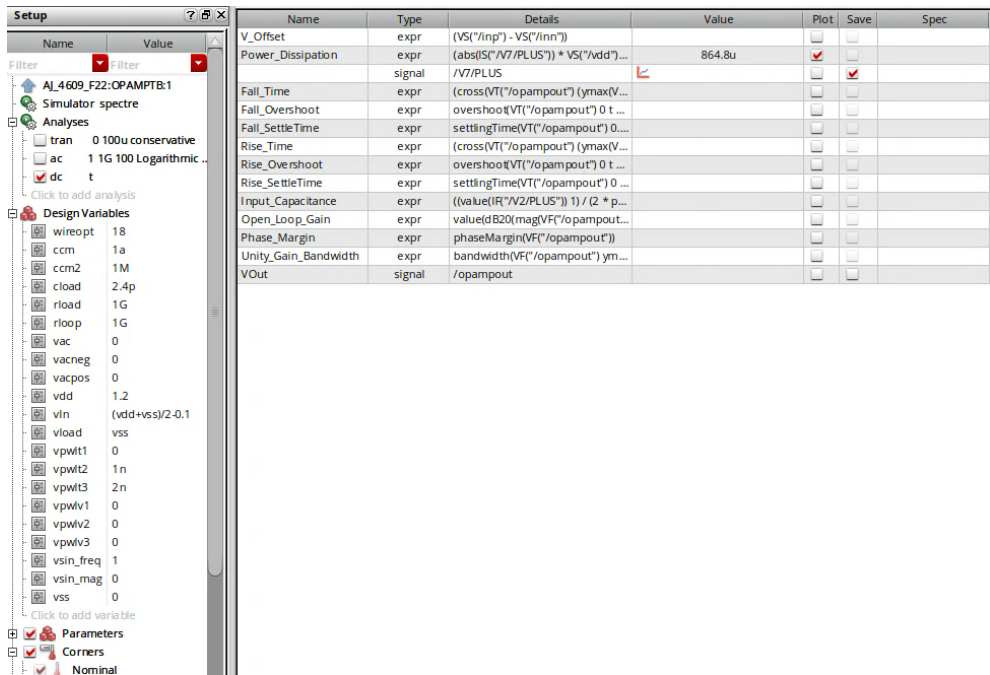


Figure 3.7: Power dissipation under normal conditions.

Voffset:  
19.19mV

Setup							
Name	Value	Name	Type	Details	Value	Plot	Save
Filter		V_Offset	expr	(VS("/inp") - VS("/inn"))	19.19m	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Filter		Power_Dissipation	expr	(abs(S("/V7/PLUS")) * VS("/vdd"))...		<input type="checkbox"/>	<input type="checkbox"/>
Filter			signal	/V7/PLUS		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_Time	expr	(cross(VT("/opampout")) (ymax(V...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_Overshoot	expr	overshoot(VT("/opampout") 0 t ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_SettleTime	expr	settlingTime(VT("/opampout") 0 ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_Time	expr	(cross(VT("/opampout")) (ymax(V...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_Overshoot	expr	overshoot(VT("/opampout") 0 t ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_SettleTime	expr	settlingTime(VT("/opampout") 0 ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Input_Capacitance	expr	((value(I(R"/V2/PLUS")) 1) / (2 * p...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Open_Loop_Gain	expr	value(dB20(mag(VF("/opampout"))		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Phase_Margin	expr	phaseMargin(VF("/opampout"))		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Unity_Gain_Bandwidth	expr	bandwidth(VF("/opampout") ym...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		VOut	signal	/opampout		<input type="checkbox"/>	<input type="checkbox"/>

Figure 3.8: V offset under normal conditions.

Risetime (10%-90%):  
1.277us

Setup							
Name	Value	Name	Type	Details	Value	Plot	Save
Filter		V_Offset	expr	(VS("/inp") - VS("/inn"))		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Power_Dissipation	expr	(abs(S("/V7/PLUS")) * VS("/vdd"))...		<input type="checkbox"/>	<input type="checkbox"/>
Filter			signal	/V7/PLUS		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_Time	expr	(cross(VT("/opampout")) (ymax(V...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_Overshoot	expr	overshoot(VT("/opampout") 0 t ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Fall_SettleTime	expr	settlingTime(VT("/opampout") 0 ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_Time	expr	(cross(VT("/opampout")) (ymax(V...	1.277u	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_Overshoot	expr	overshoot(VT("/opampout") 0 t ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Rise_SettleTime	expr	settlingTime(VT("/opampout") 0 ...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Input_Capacitance	expr	((value(I(R"/V2/PLUS")) 1) / (2 * p...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Open_Loop_Gain	expr	value(dB20(mag(VF("/opampout"))		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Phase_Margin	expr	phaseMargin(VF("/opampout"))		<input type="checkbox"/>	<input type="checkbox"/>
Filter		Unity_Gain_Bandwidth	expr	bandwidth(VF("/opampout") ym...		<input type="checkbox"/>	<input type="checkbox"/>
Filter		VOut	signal	/opampout		<input type="checkbox"/>	<input checked="" type="checkbox"/>

Figure 3.9: Rise time under normal conditions.



**Falltime (10%-90%):**  
192.1ns

Name	Value	Name	Type	Details	Plot	Save	Spec
AL 4609_F22:OPAMPB.1		V_Offset	expr	(V5("iinp") - V5("inn"))	<input type="checkbox"/>	<input type="checkbox"/>	
Analyses		Power_Dissipation	expr	(abs(S("N7/PLUS")) * V5("vdd"))...	<input type="checkbox"/>	<input type="checkbox"/>	
tran 0 100u conservative			signal	/N7/PLUS	<input type="checkbox"/>	<input type="checkbox"/>	
ac 1 1G 100 Logarithmic		Fall_Time	expr	(cross(VT("/opampout") (ymax(V...	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
dc t		Fall_Overshoot	expr	overshoot(VT("/opampout") 0 t ...	<input type="checkbox"/>	<input type="checkbox"/>	
Design Variables		Fall_SettleTime	expr	settlingTime(VT("/opampout") 0 ...	<input type="checkbox"/>	<input type="checkbox"/>	
wireopt 18		Rise_Time	expr	(cross(VT("/opampout") (ymax(V...	<input type="checkbox"/>	<input type="checkbox"/>	
ccm 1a		Rise_Overshoot	expr	overshoot(VT("/opampout") 0 t ...	<input type="checkbox"/>	<input type="checkbox"/>	
ccm2 1f		Rise_SettleTime	expr	settlingTime(VT("/opampout") 0 ...	<input type="checkbox"/>	<input type="checkbox"/>	
cload 2.4p		Input_Capacitance	expr	((value(R("V2/PLUS")) 1) / (2 * p...	<input type="checkbox"/>	<input type="checkbox"/>	
rload 1G		Open_Loop_Gain	expr	value(dB20(mag(VF("/opampout")...	<input type="checkbox"/>	<input type="checkbox"/>	
rloop 10m		Phase_Margin	expr	phaseMargin(VF("/opampout")...	<input type="checkbox"/>	<input type="checkbox"/>	
vac 1		Unity_Gain_Bandwidth	expr	bandwidth(VF("/opampout") ym...	<input type="checkbox"/>	<input type="checkbox"/>	
vacneg 0		VOut	signal	/opampout	<input type="checkbox"/>	<input type="checkbox"/>	
vacpos 0							
vdd 1.2							
vin 0							
vload vss							
vpw1t1 0							
vpw1t2 1n							
vpw1t3 2n							
vpw1v1 vdd							
vpw1v2 vdd							
vpw1v3 vss							
vsin_freq 1							
vsin_mag 0							
vss 0							

**Figure 3.10:** Fall time under normal conditions.

Following these results we will resimulate the PVT (Processes, Voltages, Temperatures) variations. There will be a total of 27 data points.

The naming convention goes in the following order (Process, Voltage, Temperature)

F = Fast

N=Nominal

S= slow

For Voltages:

Nominal = 1.2V, Fast = N+10% = 1.32V, Slow = N-10% = 1.08V

For Temperature:

Nominal = 25°C, Fast = -40°C, Slow = 85°C



## Fast process simulations:

### OPEN LOOP GAIN

FFF:19.22

FFN:19.26

FFS:18.95

FNF:19.22

FNN:19.26

FNS:18.95

FSF:19.22

FSN:19.26

FSS:18.95

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
19.22	19.26	18.95	19.22	19.26	18.95	19.22	19.26	18.95

Figure 3.11: Open loop gain under fast process.

MAX = 20.38 $\Omega$

MIN = 18.95 $\Omega$

### Unity Gain Bandwidth:

FFF: 2.993MHz

FFN:2.692MHz

FFS:3.198MHz

FNF:3.198MHz

FNN:2.993MHz

FNS:2.692MHz

FSF:3.198MHz

FSN:2.993MHz

FSS:2.692MHz

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
3.198M	2.993M	2.692M	3.198M	2.993M	2.692M	3.198M	2.993M	2.692M

Figure 3.12: Unity gain bandwidth under fast process.

MAX=3.198M

MIN= 2.043M

**Phase Margin:**

FFF: 106.3°

FFN:107.3°

FFS:108.3°

FNF:106.3°

FNN:107.3°

FNS:108.3°

FSF:106.3°

FSN:107.3°

FSS:108.3°

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
106.3	107.3	108.3	106.3	107.3	108.3	106.3	107.3	108.3

**Figure 3.13:** Phase margin under fast process.

MAX=110.8

MIN=106.3

**Power Dissipation:**

FFF: 1.202mW

FFN:1.205mW

FFS:1.128mW

FNF:1.202mW

FNN:1.205mW

FNS:1.128mW

FSF:1.202mW

FSN:1.205mW

FSS:1.128mW

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
1.202m	1.205m	1.128m	1.202m	1.205m	1.128m	1.202m	1.205m	1.128m

**Figure 3.14:** Power dissipation under fast process.

MAX=1.205m

MIN=864.8u

**Voffset:**

FFF: 35.02mV

FFN:34.25mV

FFS:31.64mV

FNF:35.02mV

FNN:34.25mV

FNS:31.64mV

FSF:35.02mV

FSN:34.25mV

FSS:31.64mV

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
35.02m	34.25m	31.64m	35.02m	34.25m	31.64m	35.02m	34.25m	31.64m

**Figure 3.15:** V offset under fast process.

MAX=35.02mV

MIN=19.19mV

**Risetime (10%-90%):**

FFF: 817.9ns

FFN: 681.8ns

FFS:654.1ns

FNF:817.9ns

FNN:681.8ns

FNS:654.1ns

FSF:817.9ns

FSN:681.8ns

FSS:654.1ns

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
817.9n	681.8n	654.1n	817.9n	681.8n	654.1n	817.9n	681.8n	654.1n

**Figure 3.16:** Rise time under fast process.

MAX=1.277us

MIN=654.1ns

**Falltime (10%-90%):**

FFF:120.6ns

FFN:132.5ns

FFS:155.7ns

FNF:120.6ns



















FNN:132.5ns

FNS:155.7ns

FSF:120.6ns

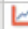FSN:132.5ns

FSS:155.7ns

FFF	FFN	FFS	FNF	FNN	FNS	FSF	FSN	FSS
Filter 	Filter 	Filter 	Filter 	Filter 	Filter 	Filter 	Filter 	Filter 
120.6n	132.5n	155.7n	120.6n	132.5n	155.7n	120.6n	132.5n	155.7n
								

**Figure 3.17:** Fall time under fast process.

MAX= 192.1ns

MIN= 120.6ns

## NOMINAL PROCESS SIMULATIONS: OPEN LOOP GAIN

NFF: 20.23

NFN: 20.36

NFS:20.55

NNF:20.23

NNN:20.36

NNS:20.55

NSF:20.23

NSN:20.36

NSS:20.55

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
20.23	20.36	20.55	20.23	20.36	20.55	20.23	20.36	20.55

**Figure 3.18:** Open loop gain under nominal process.

MAX =20.55

MIN =20.23

## Unity Gain Bandwidth:

NFF:2.173MHz

NFN: 2.034MHz

NFS:1.842MHz

NNF:2.173MHz

NNN:2.034MHz

NNS:1.842MHz

NSF:2.173MHz

NSN:2.034MHz

NSS:1.842MHz

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
2.173M	2.034M	1.842M	2.173M	2.034M	1.842M	2.173M	2.034M	1.842M

**Figure 3.19:** Unity gain bandwidth under nominal process.

MAX=2.173MHz

MIN=1.842MHz

**Phase Margin:**

NFF: 110.9°

NFN: 111.1°

NFS: 111.9°

NNF: 110.9°

NNN: 111.1°

NNS: 111.9°

NSF: 110.9°

NSN: 111.1°

NSS: 111.9°

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
110.9	111.1	111.9	110.9	111.1	111.9	110.9	111.1	111.9

**Figure 3.20:** Phase margin under nominal process.

MAX=111.9°

MIN=110.8°

**Power Dissipation::**

NFF: 858.8uW

NFN: 859uW

NFS: 791.4uW

NNF: 858.8uW

NNN: 859uW

NNS: 791.4uW

NSF: 858.8uW

NSN: 859uW

NSS: 791.4uW

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
858.8u	859u	791.4u	858.8u	859u	791.4u	858.8u	859u	791.4u

**Figure 3.21:** Power dissipation under nominal process.

MAX=864.8uW

MIN=791.4uW



**Voffset:**

NFF: 18.32mV  
 NFN: 18.9mV  
 NFS: 17.66mV  
 NNF: 18.32mV  
 NNN: 18.9mV  
 NNS: 17.66mV  
 NSF: 18.32mV  
 NSN: 18.9mV  
 NSS: 17.66mV

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
18.32m	18.9m	17.66m	18.32m	18.9m	17.66m	18.32m	18.9m	17.66m

**Figure 3.22:** V offset under nominal process.

MAX=19.19mV  
 MIN=17.66mV

**Risetime (10%-90%):**

NFF: 1.584us  
 NFN: 1.294us  
 NFS: 1.201us  
 NNF: 1.584us  
 NNN: 1.294us  
 NNS: 1.201us  
 NSF: 1.584us  
 NSN: 1.294us  
 NSS: 1.201us

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
1.584u	1.294u	1.201u	1.584u	1.294u	1.201u	1.584u	1.294u	1.201u

**Figure 3.23:** Rise time under nominal process.

MAX=1.584us  
 MIN=1.201us

### Falltime (10%-90%):

NFF: 188.5ns

NFN:193.2ns

NFS:225.5ns

NNF:188.5ns

NNN:193.2ns

NNS:225.5ns

NSF:188.5ns

NSN:193.2ns

NSS:225.5ns

NFF	NFN	NFS	NNF	NNN	NNS	NSF	NSN	NSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
188.5n	193.2n	225.5n	188.5n	193.2n	225.5n	188.5n	193.2n	225.5n

**Figure 3.24:** Fall time under nominal process.

MAX= 225.5ns

MIN=188.5ns

## SLOW process simulations:

### OPEN LOOP GAIN

SFF:20.85

SFN:20.94

SFS:21.25

SNF:20.85

SNN:20.94

SNS:21.25

SSF:20.85

SSN:20.94

SSS:21.25

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
20.85	20.94	21.25	20.85	20.94	21.25	20.85	20.94	21.25

Figure 3.25: Open loop gain under slow process.

Max =21.25

MIN = 20.38

### Unity Gain Bandwidth:

SFF:1.887MHz

SFN:1.526MHz

SFS:1.369MHz

SNF:1.887MHz

SNN:1.526MHz

SNS:1.369MHz

SSF:1.887MHz

SSN:1.526MHz

SSS:1.369MHz

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
1.887M	1.526M	1.369M	1.887M	1.526M	1.369M	1.887M	1.526M	1.369M

Figure 3.26: Unity gain bandwidth under slow process.

MAX=2.043MHz

MIN=1.369MHz

**Phase Margin:**

SFF:133.4°

SFN:125.5°

SFS:124.2°

SNF:133.4°

SNN:125.5°

SNS:124.2°

SSF:133.4°

SSN:125.5°

SSS:124.2°

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
133.4	125.5	124.2	133.4	125.5	124.2	133.4	125.5	124.2

**Figure 3.27:** Phase margin under slow process.

MAX=133.4°

MIN=110.8°

**Power Dissipation:**

SFF:604.5uW

SFN:613.8uW

SFS:565.3uW

SNF:604.5uW

SNN:613.8uW

SNS:565.3uW

SSF:604.5uW

SSN:613.8uW

SSS:565.3uW

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
604.5u	613.8u	565.3u	604.5u	613.8u	565.3u	604.5u	613.8u	565.3u

**Figure 3.28:** Power dissipation under slow process.

MAX=864.8uW

MIN=565.3uW

**Voffset:**

SFF:8.811mV

SFN:10.01mV

SFS:9.705mV

SNF:8.811mV

SNN:10.01mV

SNS:9.705mV

SSF:8.811mV

SSN:10.01mV

SSS:9.705mV

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
8.811m	10.01m	9.705m	8.811m	10.01m	9.705m	8.811m	10.01m	9.705m

**Figure 3.29:** V offset under slow process.

MAX=19.19mV

MIN=8.811mV

**Risetime (10%-90%):**

SFF:2.802us

SFN:2.261us

SFS:1.993us

SNF:2.802us

SNN:2.261us

SNS:1.993us

SSF:2.802us

SSN: 2.261us

SSS: 1.993us

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
2.802u	2.261u	1.993u	2.802u	2.261u	1.993u	2.802u	2.261u	1.993u

**Figure 3.30:** Rise time under slow process.

MAX= 2.802us

MIN= 1.277us

**Falltime (10%-90%):**

SFF: 285.6ns

SFN: 280.2ns

SFS: 317.9ns

SNF: 285.6ns

SNN: 280.2ns

SNS: 317.9ns

SSF:285.6ns

SSN: 280.2ns

SSS:317.9ns

SFF	SFN	SFS	SNF	SNN	SNS	SSF	SSN	SSS
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
285.6n	280.2n	317.9n	285.6n	280.2n	317.9n	285.6n	280.2n	317.9n

**Figure 3.31:** Fall time under slow process.

Max = 317.9ns

MIN = 192.1ns



### 3.0 OP-AMP LAYOUT

Initially, we start by sectioning off the initial op-amp design based on restrictions. This will allow us to separate the given schematic into rows which we can create in layout.

The restrictions we must keep in mind:

PMOS transistors cannot be grouped with NMOS transistors. Inputs should remain paired therefore Q1 and Q2 must remain together. The output buffer should be either grouped or close together therefore Q8 and Q9 must be sectioned off. The differential-input first stage should remain together Q3 must remain with Q4. Finally The bias circuitry must remain together in one row therefore Q14, Q12, Q15 and Q13 should remain together.

Based on these restrictions the op-amp was sectioned off into the four groups shown in the diagram below:

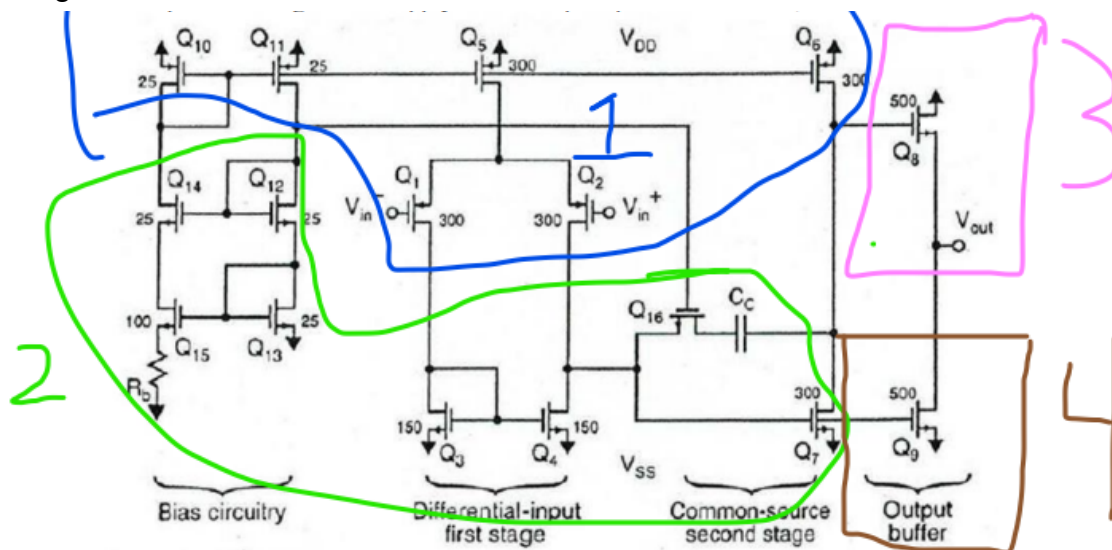


Figure 3.32: Op-Amp Layout Floor-plan sectioning

We decided to keep the PMOS transistors in one group following this we sectioned the current mirrors into the second group. Finally since transistors 3 and 4 have a large amount of fingers we split them into their own individual rows creating 4 rows in total.

Next, we must calculate the W/L ratios and decide on the amount of fingers as well as the individual finger width.

Total finger calculation for ROW 1 = Q1 + Q2 + Q5 + Q6 + Q10 + Q11 + . First we must decide on the width of the individual fingers should they be on the same row. Q10 and Q11 have a width of 1um therefore we must make the widths of the individual fingers of Q1, Q2, Q5 and Q6 the same size. Since they use the same finger width and amount of

fingers we can change the amount of fingers to 12 and therefore will have the same width.

The total amount of fingers =  $(12 \times 4) + 2 = 50$ .

For the third and fourth row since they have the same amount of fingers and width then we are able to calculate how many fingers are needed to stay consistent. We opted to keep them at 50 fingers to remain symmetrical with row 1.

Now for row 2 we have gates  $Q3 + Q4 + Q7 + Q16 + Q12 + Q13 + Q14 + Q15$ . In this case we want to keep the width the same at 1um. Based on that we must change the amount of fingers to keep that constraint.

Based on the calculations done the new finger amounts become  
 $Q3=Q4=6, Q16=1, Q7=12, Q14=Q12=Q13=1, Q15 = 4$

Now calculating the total amount of fingers:

$Q3 + Q4 + Q16 + Q7 + Q14 + Q12 + Q13 + Q15$

$= 6 + 6 + 1 + 12 + 3 + 4$

$= 32$

To remain consistent we must add a minimum of 20 dummies.

Finally, we layout the calculated fingers symmetrically around the centre placing dummies to both keep the amount of fingers consistent while also ensuring two transistors that do not share a common source net are not placed together. Based on the dummies added the total amount of fingers was changed to 54. Therefore each row has a total of 54 transistors and dummies.

#### Layout Floor Plan

0 = 10, Z = 11, D = Dummy

66 55 66 55 66 55 D 11 22 11 22 11 22 D 0	Z D 22 11 22 11 22 11 D 55 66 55 66 55 66
---	---

D 88 99 88 99 88 99 88 99 88 99 88 99 88	99 88 99 88 99 88 99 88 99 88 99 88 99 D
--	--


D 88 99 88 99 88 99 88 99 88 99 88 99 88	99 88 99 88 99 88 99 88 99 88 99 88 99 D
--	--

12=A, 13 = B, 14=C, 15= X, 16=Y

DDDDDDDDD 77 77 77 D 33 44 33 D XX CD	A D XX D B D 44 33 44 DY D77 7777DDDDD
---------------------------------------	--

## 4.0 LAYOUT SIMULATION

Figure 3.33 below shows the final OP-AMP layout design. It matches the layout floor plan shown above.

 

**Figure 3.33:** OpAmp layout design.

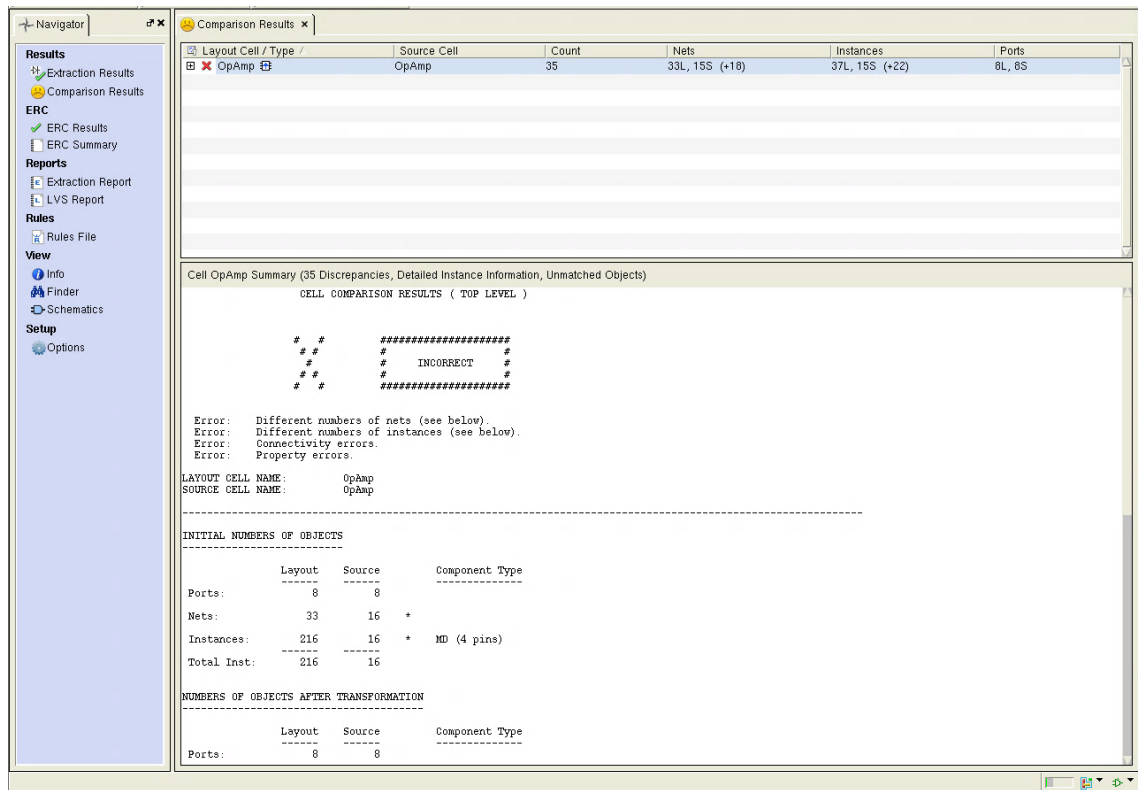


Figure 3.34: Layout LVS

Unfortunately, we were unable to fix all LVS errors and as a result couldn't run the required simulations.

## **Chapter 4: Group Member Contributions**

### **1.0 CuSOI Schematics & Simulation:**

Hussin Created the schematics and testbenches for the XNOR\_RESET, Oscillator, D-flip-Flop, Output-Driver and the full top level static PRSG. Theo created the schematics and testbenches for the NAND gate, NOR gate, PRSG, and Input-Protection.

However, since the top level test-bench for the entire static PRSG was more difficult than anticipated, Theo helped in the creation of the testbench.

### **2.0 CuSOI Layout**

Hussin and Theo both worked on the creation of the individual logic gates NAND and NOR. Hussin created the initial layout, and Theo utilised them to create a more space efficient version. Hussin created the layout for the input-protection, output-driver, oscillator and PRSG. Theo created the D-FlipFlop, XNOR\_Reset and inverter. Although the overall top level full static PRSG was completed by both, Theo provided more input and took the lead towards its connections and completion.

### **3.0 CuSOI Report**

The CuSOI report was almost entirely done by Theo with Hussin adding references and images where required as well as cleaning it, editing, and adding figure numbers prior to submission.

### **4.0 OpAmp Schematics & OpAmp PVT Simulations**

The opAmp schematic and PVT simulations were done mostly by Hussin Abdullah with Theo providing input and help whenever needed

### **5.0 OpAmp Layout**

The top level layout floor plan was created entirely by Hussin with theo providing input and assistance whenever required. The overall layout was completed by Theo with Hussin providing input and help whenever required.

### **6.0 OpAmp Report**

The OpAmp report was written entirely by Hussin Abdullah

### **7.0 General Report Writing**

The report was split evenly with editing and figures added by both figures.



## APPENDIX:

### 1. STATIC PRSG final DRC for Layout:

```
--- RULECHECK RESULTS STATISTICS
---
RULECHECK METAL_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK METAL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK POLY_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK POLY_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK FIELD_POLY_DWELL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK FIELD_POLY_SOURCE_DRAIN_TOUCHING ... TOTAL Result Count = 0 (0)
RULECHECK DWELL_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK DWELL_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_WIDTH ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_METAL_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_POLY_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK CHANNEL_CONTACT_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK CONTACT_D_WELL_OVERLAP ..... TOTAL Result Count = 0 (0)
RULECHECK NWELL_DWELL_OVERLAP.1 ..... TOTAL Result Count = 0 (0)
RULECHECK NWELL_DWELL_OVERLAP.2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_NWELL_OVERLAP.2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_P_SOURCE_DRAIN_ENCLOSURE ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_DWELL_OVERLAP.2 ..... TOTAL Result Count = 0 (0)
RULECHECK Pplus_N_SOURCE_DRAIN_SPACING ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE.1 ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE.2 ..... TOTAL Result Count = 0 (0)
RULECHECK BAD_GATE.3 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.1 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.2 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.3 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.4 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.5 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.6 ..... TOTAL Result Count = 0 (0)
RULECHECK Grid.7 ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_METAL ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_POLY ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_DWELL ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_NPLUS ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_PPLUS ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_CONTACT ..... TOTAL Result Count = 0 (0)
RULECHECK ART_TO_NWELL ..... TOTAL Result Count = 0 (0)
-----
--- RULECHECK RESULTS STATISTICS (BY CELL)
---
-----
--- SUMMARY
---
TOTAL CPU Time: 0
TOTAL REAL Time: 0
TOTAL Original Layer Geometries: 747 (2145)
TOTAL DRC RuleChecks Executed: 36
TOTAL DRC Results Generated: 0 (0)
```

---

## 2. Static PRSG final LVS report for Layout:

The screenshot shows the 'Results' window of Calibre, displaying the 'LVS Report' for the 'TOP\_HT' cell. The report is titled 'Cell TOP\_HT Summary (Clean)' and 'CELL COMPARISON RESULTS ( TOP LEVEL )'. It shows a comparison between the 'LAYOUT CELL NAME' and the 'SOURCE CELL NAME', both of which are 'TOP\_HT'. The report indicates that the comparison is 'CORRECT'.

Layout Cell / Type	Source Cell	Nets	Instances	Ports
TOP_HT	TOP_HT	63L, 63S	63L, 63S	7L, 7S

Cell TOP\_HT Summary (Clean)

CELL COMPARISON RESULTS ( TOP LEVEL )

#####  
# CORRECT #  
#####

LAYOUT CELL NAME: TOP\_HT  
SOURCE CELL NAME: TOP\_HT

## 3. OP AMP DRC for LAYOUT

The screenshot shows the 'Calibre - RVE v2019.1\_18.11 : OpAmp.drc.results' window. The window displays the 'Check / Cell' list on the left, with 'Check LAYOUT\_INPUT' selected. The main area shows 'No Results Found'.

Calibre - RVE v2019.1\_18.11 : OpAmp.drc.results

File View Highlight Tools Window Setup Help

Show All No Results Found

Check / Cell  
Check LAYOUT\_INPUT

#### 4. OP AMP final LVS report for layout:

The screenshot displays the 'Comparison Results' window of a CAD application. The left sidebar contains a 'Navigator' pane with sections for Results, ERC, Reports, Rules, and View. The main area shows a table of comparison results for the 'OpAmp' cell.

Layout Cell / Type	Source Cell	Count	Nets	Instances	Ports
OpAmp	OpAmp	35	33L, 15S (+18)	37L, 15S (+22)	8L, 8S

Below the table, a 'Cell OpAmp Summary (35 Discrepancies, Detailed Instance Information, Unmatched Objects)' is provided. It includes a 'CELL COMPARISON RESULTS ( TOP LEVEL )' section with a summary of errors:

```

#####
# #      #
# #      # INCORRECT #
# #      #
# #      #
#####
Error: Different numbers of nets (see below).
Error: Different numbers of instances (see below).
Error: Connectivity errors.
Error: Property errors.

```

It also lists the layout and source cell names, followed by a table of initial numbers of objects:

	Layout	Source	Component Type
Ports:	8	8	
Nets:	33	16	*
Instances:	216	16	* MD (4 pins)
Total Inst:	216	16	

Finally, it shows a table of numbers of objects after transformation:

	Layout	Source	Component Type
Ports:	8	8	